

EXAMPLE 36.1 Finding resistor voltages

In the circuit of **FIGURE 36.6**, what are (a) the peak voltage across each resistor and (b) the instantaneous resistor voltages at $t = 20$ ms?


VISUALIZE Figure 36.6 shows the circuit diagram. The two resistors are in series.

SOLVE a. The equivalent resistance of the two series resistors is $R_{\text{eq}} = 5 \Omega + 15 \Omega = 20 \Omega$. The instantaneous current through the equivalent resistance is

$$i_R = \frac{v_R}{R_{\text{eq}}} = \frac{\mathcal{E}_0 \cos \omega t}{R_{\text{eq}}} = \frac{(100 \text{ V}) \cos(2\pi(60 \text{ Hz})t)}{20 \Omega} \\ = (5.0 \text{ A}) \cos(2\pi(60 \text{ Hz})t)$$

The peak current is $I_R = 5.0$ A, and this is also the peak current through the two resistors that form the 20Ω equivalent resistance. Hence the peak voltage across each resistor is

$$V_R = I_R R = \begin{cases} 25 \text{ V} & 5 \Omega \text{ resistor} \\ 75 \text{ V} & 15 \Omega \text{ resistor} \end{cases}$$

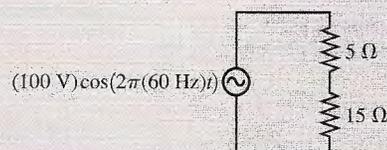FIGURE 36.6 An AC resistor circuit.

b. The instantaneous current at $t = 0.020$ s is

$$i_R = (5.0 \text{ A}) \cos(2\pi(60 \text{ Hz})(0.020 \text{ s})) = 1.55 \text{ A}$$


The resistor voltages at this time are

$$v_R = i_R R = \begin{cases} 7.7 \text{ V} & 5 \Omega \text{ resistor} \\ 23.2 \text{ V} & 15 \Omega \text{ resistor} \end{cases}$$

ASSESS The sum of the instantaneous voltages, 30.9 V, is what you would find by calculating \mathcal{E} at $t = 20$ ms. This self-consistency gives us confidence in the answer.

STOP TO THINK 36.1 The resistor whose voltage and current phasors are shown here has resistance R

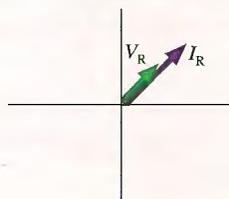- $> 1 \Omega$
- $< 1 \Omega$
- It's not possible to tell.



36.2 Capacitor Circuits

FIGURE 36.7a shows current i_C charging a capacitor with capacitance C . The instantaneous capacitor voltage is $v_C = q/C$, where $\pm q$ is the charge on the two capacitor plates at this instant of time. It is useful to compare Figure 36.7a to Figure 36.3 for a resistor.

FIGURE 36.7b, where capacitance C is connected across an AC source of emf \mathcal{E} , is the most basic capacitor circuit. The capacitor is in parallel with the source, so the capacitor voltage equals the emf: $v_C = \mathcal{E} = \mathcal{E}_0 \cos \omega t$. It will be useful to write

$$v_C = V_C \cos \omega t \quad (36.6)$$

where V_C is the peak or maximum voltage across the capacitor. You can see that $v_C = \mathcal{E}_0$ in this single-capacitor circuit.

To find the current to and from the capacitor, we first write the charge

$$q = Cv_C = CV_C \cos \omega t \quad (36.7)$$

The current is the *rate* at which charge flows through the wires, $i_C = dq/dt$, thus

$$i_C = \frac{dq}{dt} = \frac{d}{dt}(CV_C \cos \omega t) = -\omega CV_C \sin \omega t \quad (36.8)$$

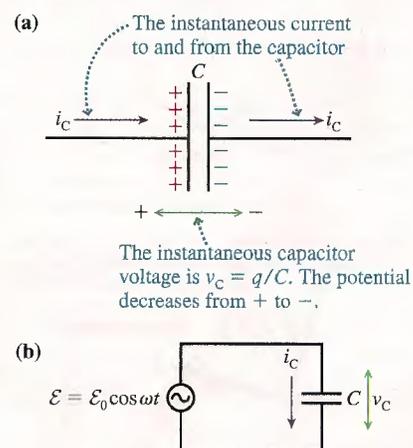
FIGURE 36.7 An AC capacitor circuit.

FIGURE 36.8 Graph and phasor diagrams of the capacitor current and voltage.


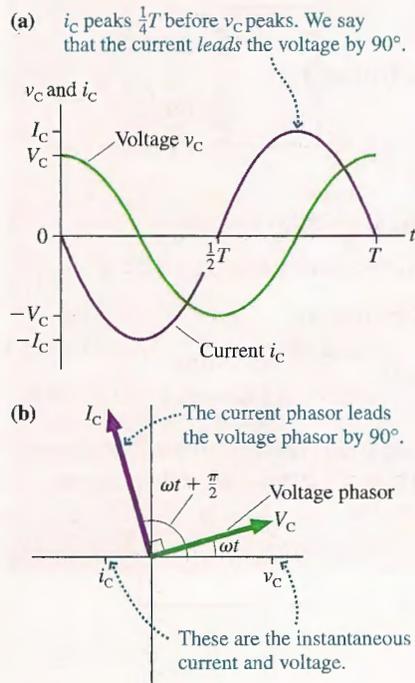


FIGURE 36.9 In a mechanical analogy, the velocity of a simple harmonic oscillator leads the position by 90° .

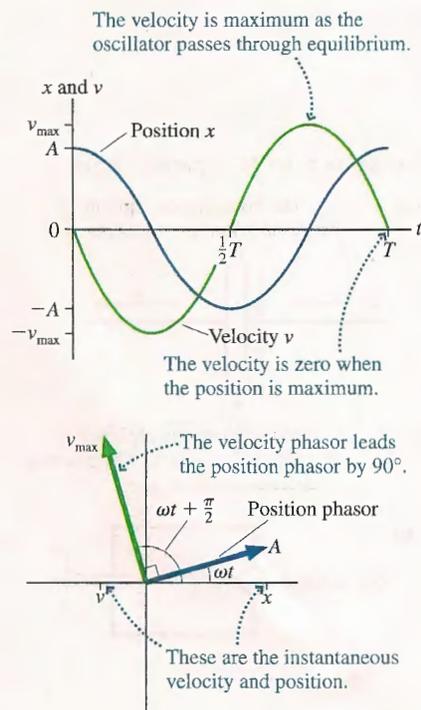

We can most easily see the relationship between the capacitor voltage and current if we use the trigonometric identity $-\sin(x) = \cos(x + \pi/2)$ to write

$$i_C = \omega C V_C \cos\left(\omega t + \frac{\pi}{2}\right) \quad (36.9)$$

In contrast to a resistor, a capacitor's current and voltage are *not* in phase. In **FIGURE 36.8a**, a graph of the instantaneous voltage v_C and current i_C , you can see that the current peaks one-quarter of a period *before* the voltage peaks. The phase angle of the current phasor on the phasor diagram of **FIGURE 36.8b** is $\pi/2$ rad—a quarter of a circle—larger than the phase angle of the voltage phasor.

We can summarize this finding:

The AC current to and from a capacitor leads the capacitor voltage by $\pi/2$ rad, or 90° .

The current reaches its peak value I_C at the instant the capacitor is fully discharged and $v_C = 0$. The current is zero at the instant the capacitor is fully charged. You saw a similar behavior in the oscillation of an LC circuit in Chapter 34.

A simple harmonic oscillator provides a mechanical analogy of the 90° phase difference between current and voltage. You learned in Chapter 14 (refer to Section 14.1 and Figure 14.5) that the position and velocity of a simple harmonic oscillator are

$$x = A \cos \omega t$$

$$v = \frac{dx}{dt} = -\omega A \sin \omega t = -v_{\max} \sin \omega t = v_{\max} \cos\left(\omega t + \frac{\pi}{2}\right)$$

You can see in **FIGURE 36.9** that the velocity leads the position by 90° in the same way that the capacitor current (which is proportional to the charge velocity) leads the voltage.

Capacitive Reactance

We can use Equation 36.9 to see that the peak current to and from a capacitor is $I_C = \omega C V_C$. This relationship between the peak voltage and peak current looks much like Ohm's law for a resistor if we define the **capacitive reactance** X_C to be

$$X_C \equiv \frac{1}{\omega C} \quad (36.10)$$

With this definition,

$$I_C = \frac{V_C}{X_C} \quad \text{or} \quad V_C = I_C X_C \quad (36.11)$$

The units of reactance, like those of resistance, are ohms.

NOTE ▶ Reactance relates the *peak* voltage V_C and current I_C . But reactance differs from resistance in that it does *not* relate the instantaneous capacitor voltage and current because they are out of phase. That is, $v_C \neq i_C X_C$. ◀

A resistor's resistance R is independent of the emf frequency. In contrast, as **FIGURE 36.10** shows, a capacitor's reactance X_C depends inversely on the frequency. The reactance becomes very large at low frequencies (i.e., the capacitor is a large impediment to current). This makes sense because $\omega = 0$ would be a nonoscillating DC cir-

EXAMPLE 36.4 Designing a filter

For a science project, you've built a radio to listen to AM radio broadcasts at frequencies near 1 MHz. The basic circuit is an antenna, which produces a very small oscillating voltage when it absorbs the energy of an electromagnetic wave, and an amplifier. Unfortunately, your neighbor's short-wave radio broadcast at 10 MHz interferes with your reception. Having just finished physics, you decide to solve this problem by placing a filter between the antenna and the amplifier. You happen to have a 500 pF capacitor. What frequency should you select as the filter's crossover frequency? What value of resistance will you need to build this filter?

MODEL You need a low-pass filter to block signals at 10 MHz while passing the lower-frequency AM signal at 1 MHz.

VISUALIZE The circuit will look like the low-pass filter in Figure 36.13a. The oscillating voltage generated by the antenna will be the emf, and v_{out} will be sent to the amplifier.


SOLVE You might think that a crossover frequency near 5 MHz, about halfway between 1 MHz and 10 MHz, would work best. But 5 MHz is a factor of 5 higher than 1 MHz while only a factor of 2 less than 10 MHz. A crossover frequency the same factor above 1 MHz as it is below 10 MHz will give the best results. In practice, choosing $f_c = 3$ MHz would be sufficient. You can then use Equation 36.15 to select the proper resistor value:

$$R = \frac{1}{\omega_c C} = \frac{1}{2\pi(3 \times 10^6 \text{ Hz})(500 \times 10^{-12} \text{ F})} = 106 \Omega \approx 100 \Omega$$

ASSESS Rounding to 100 Ω is appropriate because the crossover frequency was determined to only one significant figure. Such "sloppy design" is adequate when the two frequencies you need to distinguish are well separated.

STOP TO THINK 36.4

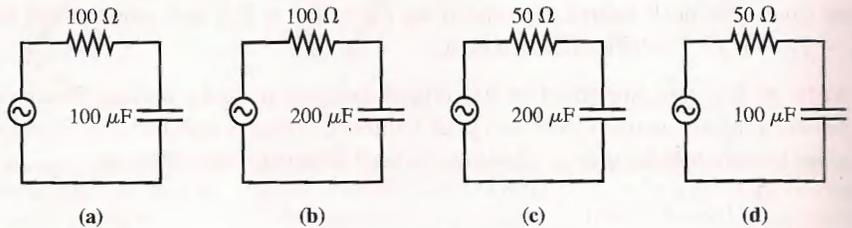
Rank in order, from largest to smallest, the crossover frequencies $(\omega_c)_a$ to $(\omega_c)_d$ of these four circuits.



36.4 Inductor Circuits

FIGURE 36.14 Using an inductor in an AC circuit.

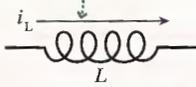(a) The instantaneous current through the inductor



The instantaneous inductor voltage is $v_L = L(di_L/dt)$.

(b)

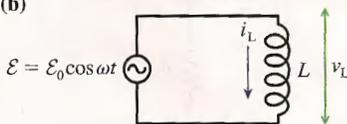


FIGURE 36.14a shows the instantaneous current i_L through an inductor. If the current is changing, the instantaneous inductor voltage is

$$v_L = L \frac{di_L}{dt} \tag{36.16}$$

You learned in Chapter 34 that the potential decreases in the direction of the current if the current is increasing ($di_L/dt > 0$) and increases if the current is decreasing ($di_L/dt < 0$).

FIGURE 36.14b is the simplest inductor circuit. The inductor L is connected across the AC source, so the inductor voltage equals the emf: $v_L = \mathcal{E} = \mathcal{E}_0 \cos \omega t$. We can write

$$v_L = V_L \cos \omega t \tag{36.17}$$

where V_L is the peak or maximum voltage across the inductor. You can see that $V_L = \mathcal{E}_0$ in this single-inductor circuit.

We can find the inductor current i_L by integrating Equation 36.17. First, use Equation 36.17 to write Equation 36.16 as

$$di_L = \frac{v_L}{L} dt = \frac{V_L}{L} \cos \omega t dt \tag{36.18}$$

Integrating gives

$$\begin{aligned}
 i_L &= \frac{V_L}{L} \int \cos \omega t dt = \frac{V_L}{\omega L} \sin \omega t = \frac{V_L}{\omega L} \cos \left(\omega t - \frac{\pi}{2} \right) \\
 &= I_L \cos \left(\omega t - \frac{\pi}{2} \right)
 \end{aligned}
 \tag{36.19}$$

where $I_L = V_L/\omega L$ is the peak or maximum inductor current.

NOTE ► Mathematically, Equation 36.19 could have an integration constant i_0 . An integration constant would represent a constant DC current through the inductor, but there is no DC source of potential in an AC circuit. Hence, on physical grounds, we set $i_0 = 0$ for an AC circuit. ◀

We define the **inductive reactance**, analogous to the capacitive reactance, to be

$$X_L = \omega L \tag{36.20}$$

Then the peak current $I_L = V_L/\omega L$ and the peak voltage are related by

$$I_L = \frac{V_L}{X_L} \quad \text{or} \quad V_L = I_L X_L \tag{36.21}$$

FIGURE 36.15 shows that the inductive reactance increases as the frequency increases. This makes sense. Faraday's law tells us that the induced voltage across a coil increases as the time rate of change of \vec{B} increases, and \vec{B} is directly proportional to the inductor current. For a given peak current I_L , \vec{B} changes more rapidly at higher frequencies than at lower frequencies, and thus V_L is larger at higher frequencies than at lower frequencies.

FIGURE 36.16a is a graph of the inductor voltage and current. You can see that the current peaks one-quarter of a period *after* the voltage peaks. The angle of the current phasor on the phasor diagram of FIGURE 36.16b is $\pi/2$ rad less than the angle of the voltage phasor. We can summarize this finding:

The AC current through an inductor lags the inductor voltage by $\pi/2$ rad, or 90° .

FIGURE 36.15 The inductive reactance as a function of frequency.


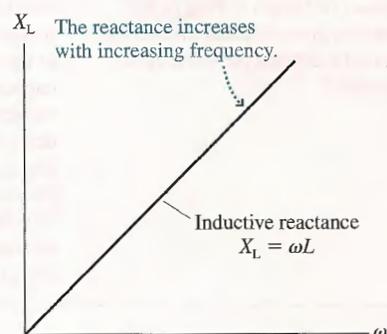


FIGURE 36.16 Graphs and phasor diagrams of the inductor current and voltage.

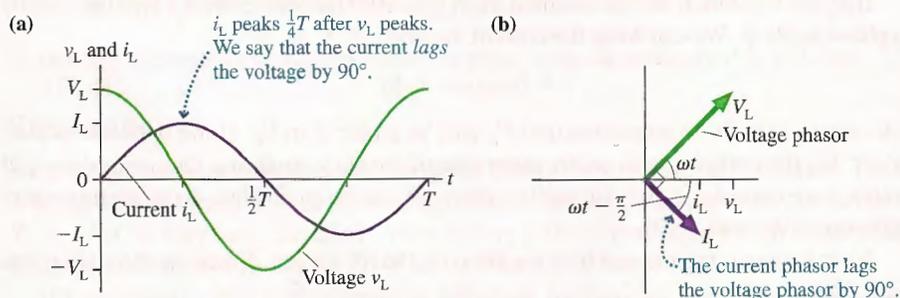

EXAMPLE 36.5 Current and voltage of an inductor

A $25 \mu\text{H}$ inductor is used in a circuit that oscillates at 100 kHz . The current through the inductor reaches a peak value of 20 mA at $t = 5.0 \mu\text{s}$. What is the peak inductor voltage, and when, closest to $t = 5.0 \mu\text{s}$, does it occur?

MODEL The inductor current lags the voltage by 90° , or, equivalently, the voltage reaches its peak value one-quarter period *before* the current.

VISUALIZE The circuit looks like Figure 36.14b.

SOLVE The inductive reactance at $f = 100 \text{ kHz}$ is

$$X_L = \omega L = 2\pi(1.0 \times 10^5 \text{ Hz})(25 \times 10^{-6} \text{ H}) = 16 \Omega$$

Thus the peak voltage is $V_L = I_L X_L = (20 \text{ mA})(16 \Omega) = 320 \text{ mV}$. The voltage peak occurs one-quarter period before the current peaks, and we know that the current peaks at $t = 5.0 \mu\text{s}$. The period of a 100 kHz oscillation is $10.0 \mu\text{s}$, so the voltage peaks at

$$t = 5.0 \mu\text{s} - \frac{10.0 \mu\text{s}}{4} = 2.5 \mu\text{s}$$