

LRC resonance circuit for week 8. $L = 22 \text{ mH}$, $R = 50 \Omega$, $C = 18 \text{ nF}$

