
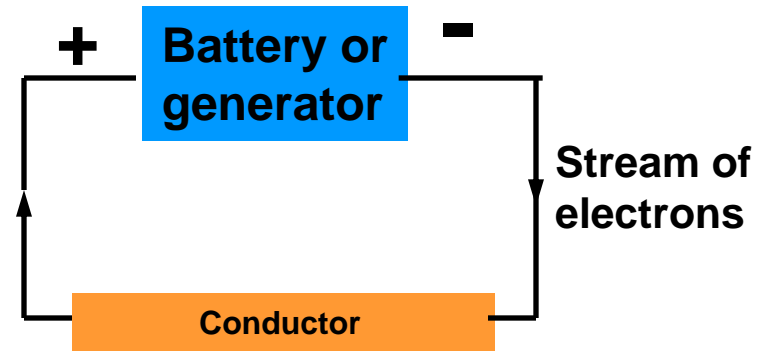


**ABOUT THE “UNSUNG HERO” OF THE  
ELECTRICITY GENERATING SYSTEM:**

# **THE GRID**

**Some analogies between the flow of current in a conductor, and the flow of water in a rigid pipe (good to keep in mind for those who are scared by “Volts”, “Amps”, “Ohms” ..):**

Pressure:

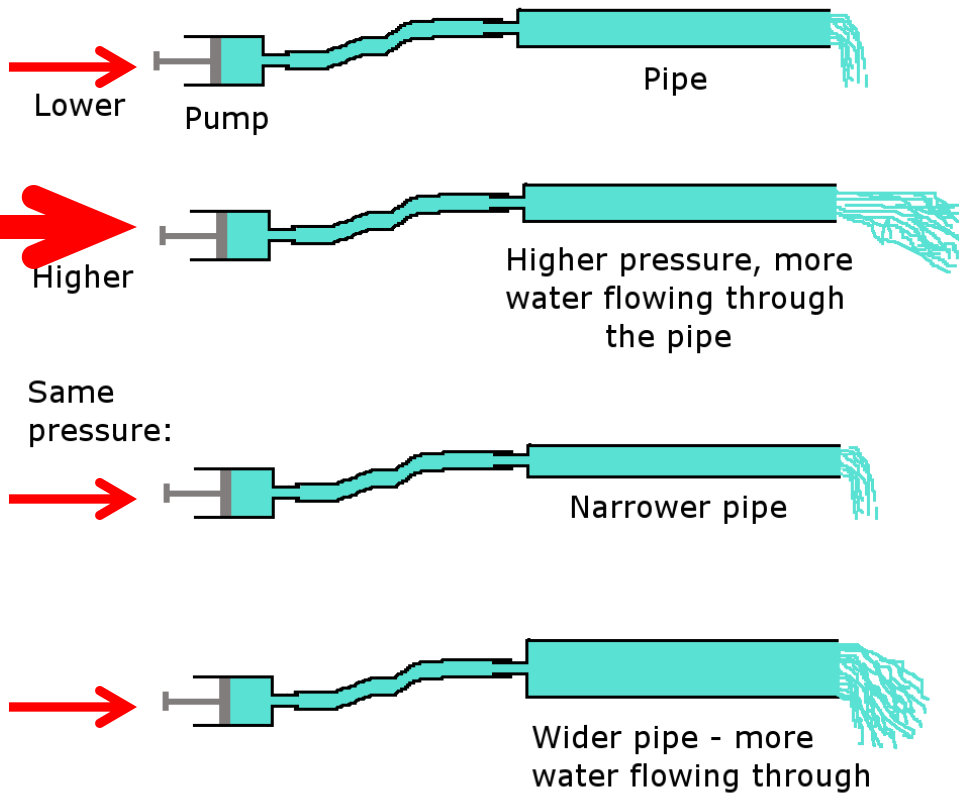

(Water pump)  $\Leftrightarrow$  (Current source)

(Pipe)  $\Leftrightarrow$  (Conductor)

(Water flow)  $\Leftrightarrow$  (Charge flow)


$\left( \begin{array}{l} \text{Water volume flowing} \\ \text{out per second} \end{array} \right) \Leftrightarrow \left( \begin{array}{l} \text{Charge flow per} \\ \text{second (Amps)} \end{array} \right)$

$\left( \begin{array}{l} \text{Pump} \\ \text{pressure} \end{array} \right) \Leftrightarrow \left( \begin{array}{l} \text{Voltage} \\ \text{applied} \end{array} \right)$

$\left( \begin{array}{l} \text{Pipe} \\ \text{"narrowness"} \end{array} \right) \Leftrightarrow \left( \begin{array}{l} \text{Conductor} \\ \text{resistance} \end{array} \right)$

## One more thing to remember:


### Rigid water pipe:

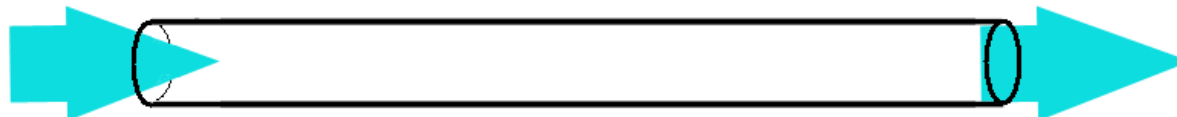

The volume flowing in = the volume flowing out

(water cannot accumulate in the pipe)

### Any conducting body:

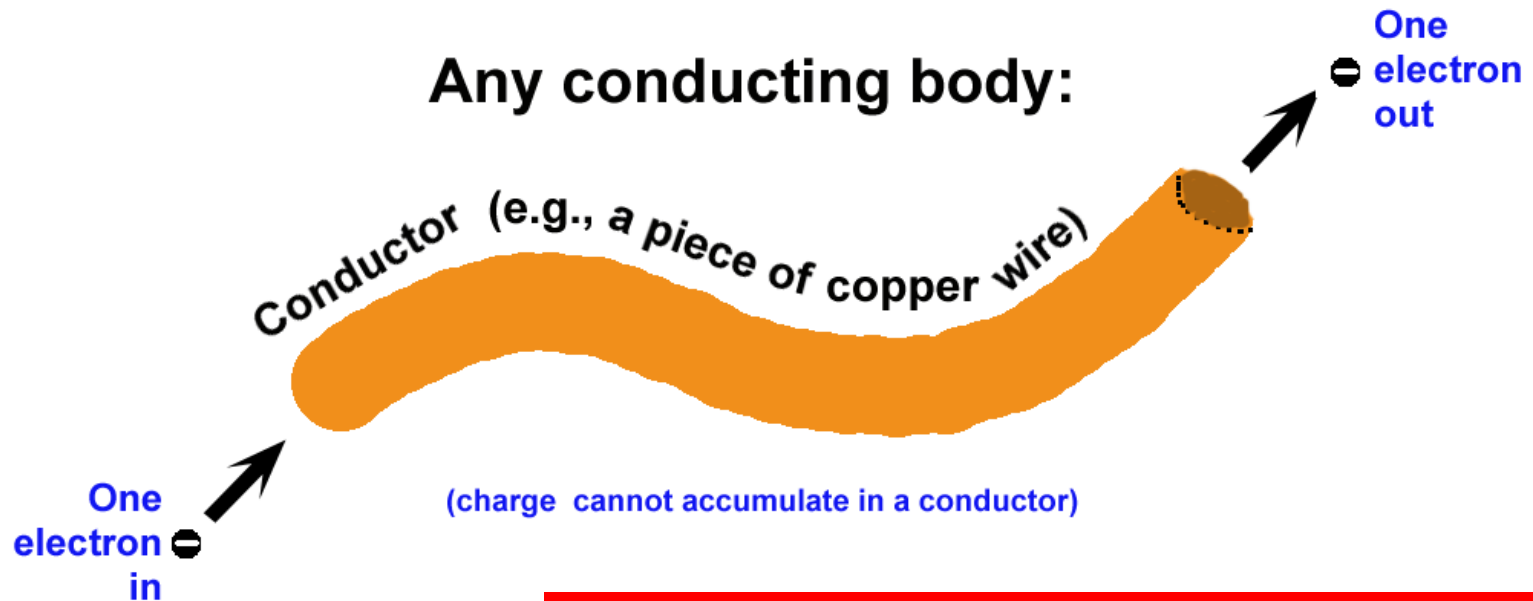

**Note: this is also true for any current source. Current not only flows out of a battery – exactly the same amount of charge returns by the other terminal.**

## Basic laws of electric current flow:


Ohm Law :  $I = \frac{V}{R}$


Work done by electric current  $I$  over a time period  $\Delta t$ :  $W = V \cdot I \cdot \Delta t$   
(converted into Joule heat).

Then, the power is :  $P = V \cdot I$

Combining with the Ohm Law, we get :

$$P = I^2 \cdot R$$

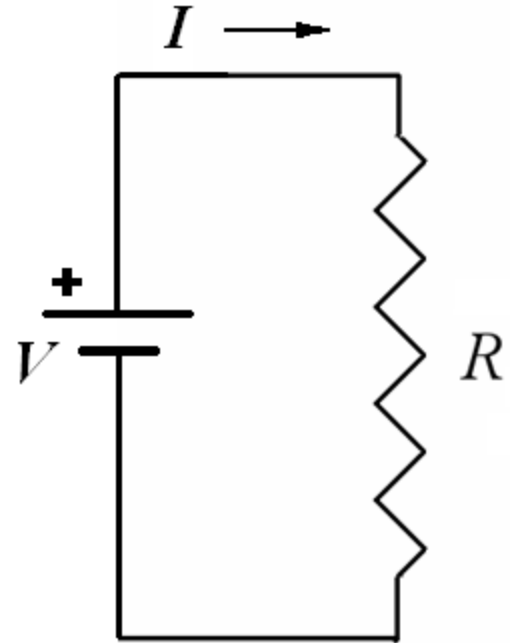

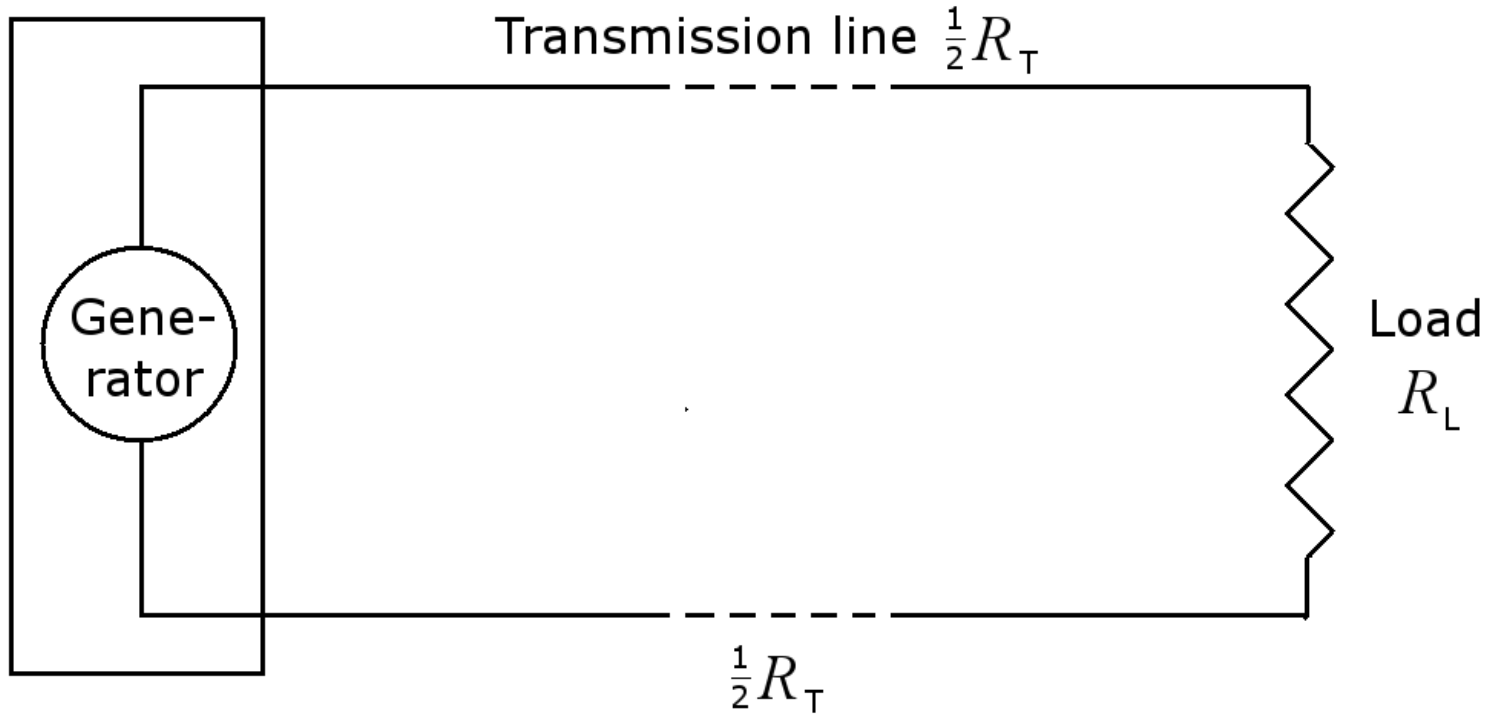

Power received :  $P_L = R_L \cdot I^2$

Power dissipated in transmission line :  $P_T = R_T \cdot I^2$

Total power send out :  $P_{\text{total}} = P_L + P_T = (R_L + R_T) \cdot I^2$


Transmission efficiency :  $\varepsilon = \frac{P_L}{P_{\text{total}}} = \frac{R_L}{R_L + R_T}$


E.g., if  $R_T = R_L$  , then 50% of power send out is "lost" in the line
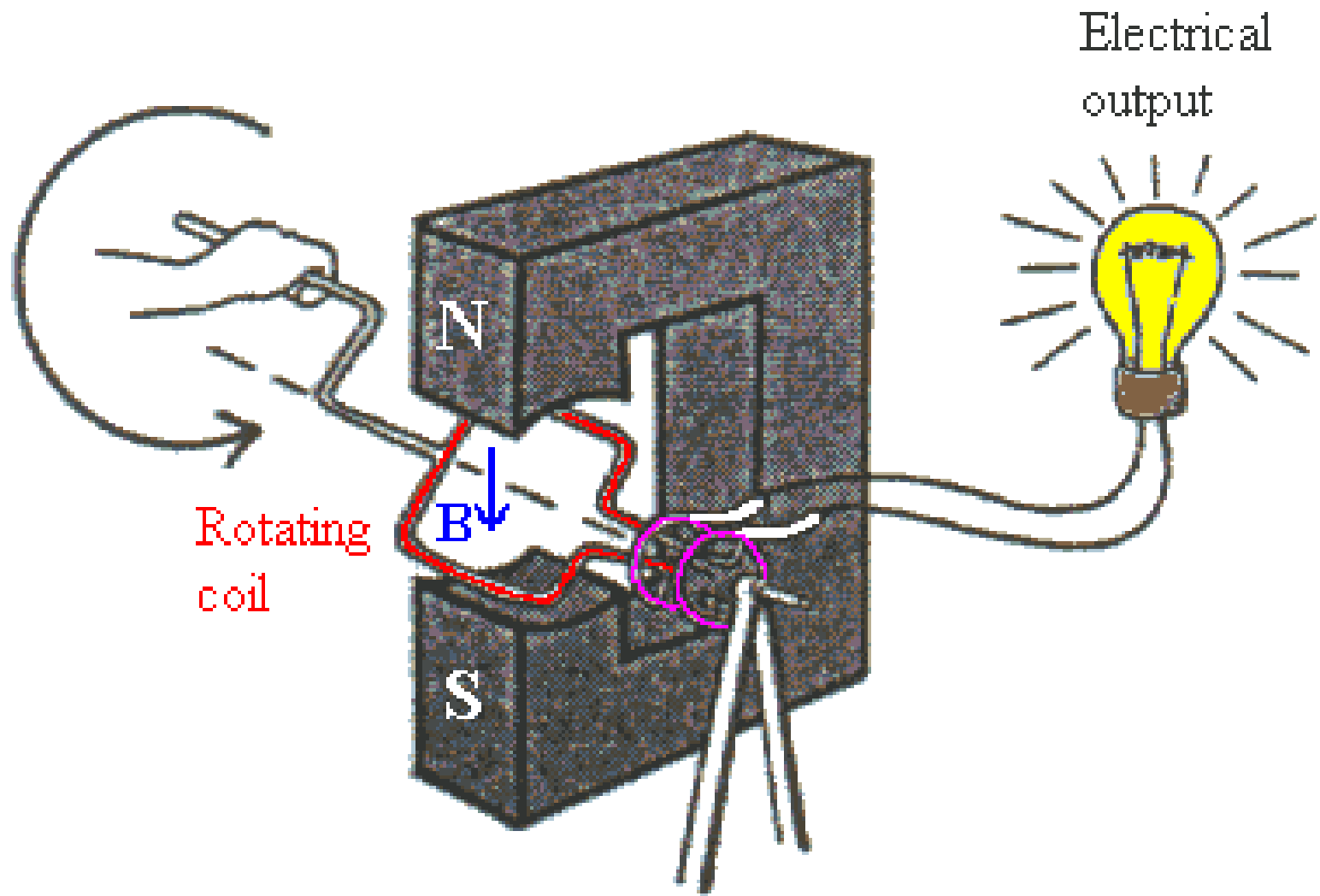
# **Wire resistance: the American Wire Gauge (AWG) standard.**

[Wire gauge chart, AWG calculator and theory.](#)


[Another AWS table & calculator, more details.](#)



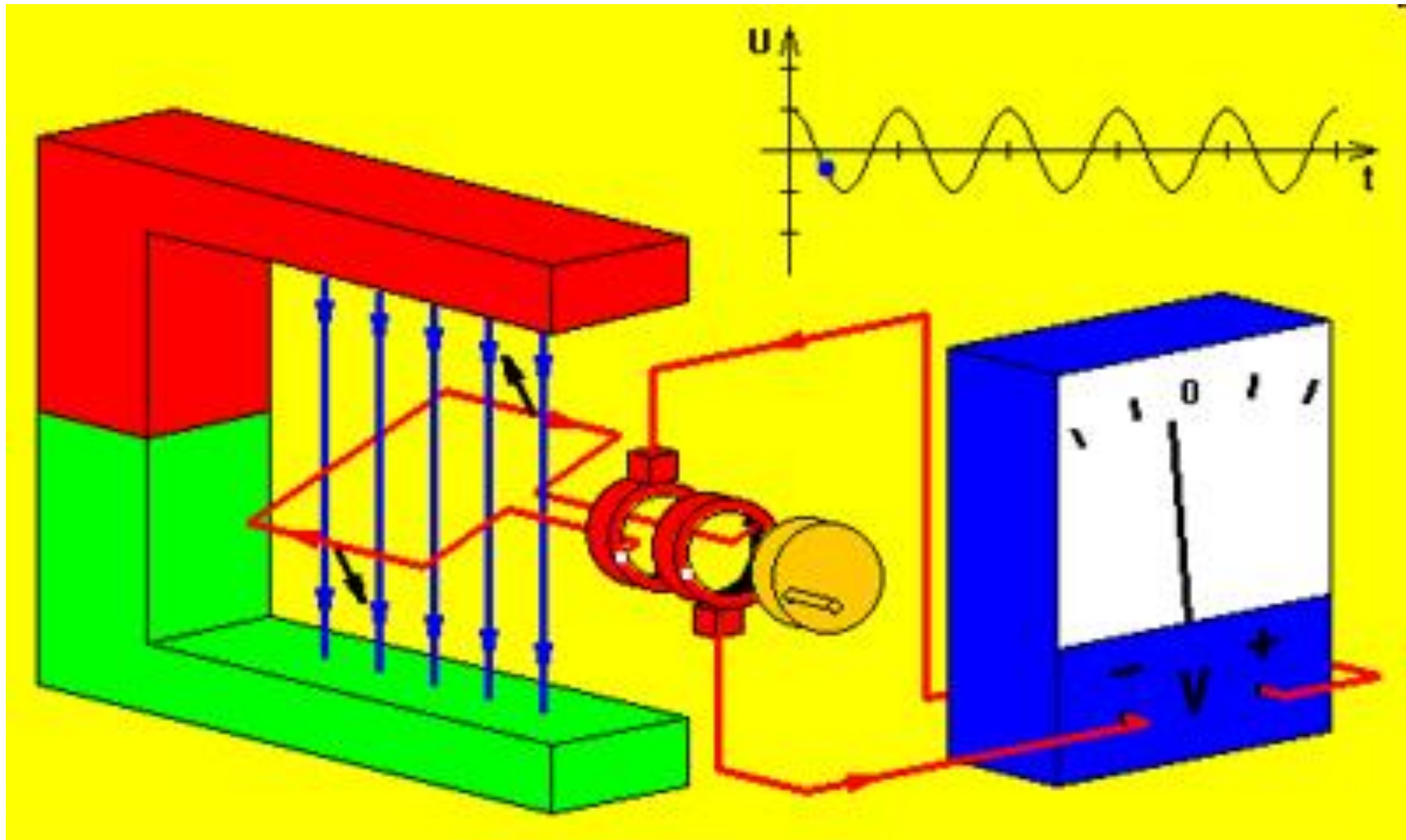



# Generator

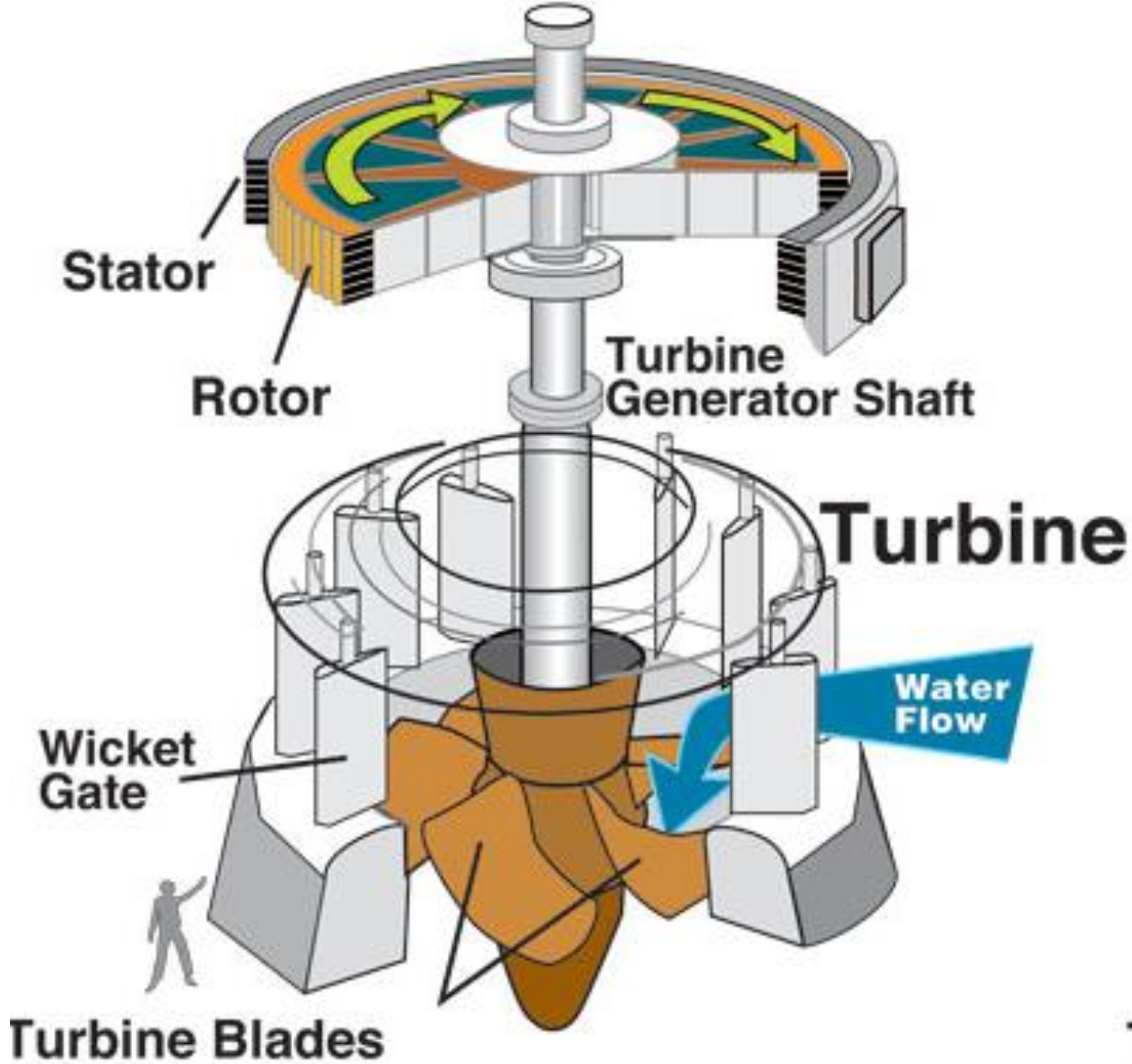

# Remedy: alternating current + transformers

**Primary winding**

$N_P$  turns

Primary current  $I_P$


Primary voltage  $V_P$

**Secondary winding**

$N_S$  turns

Secondary current  $I_S$

Secondary voltage  $V_S$

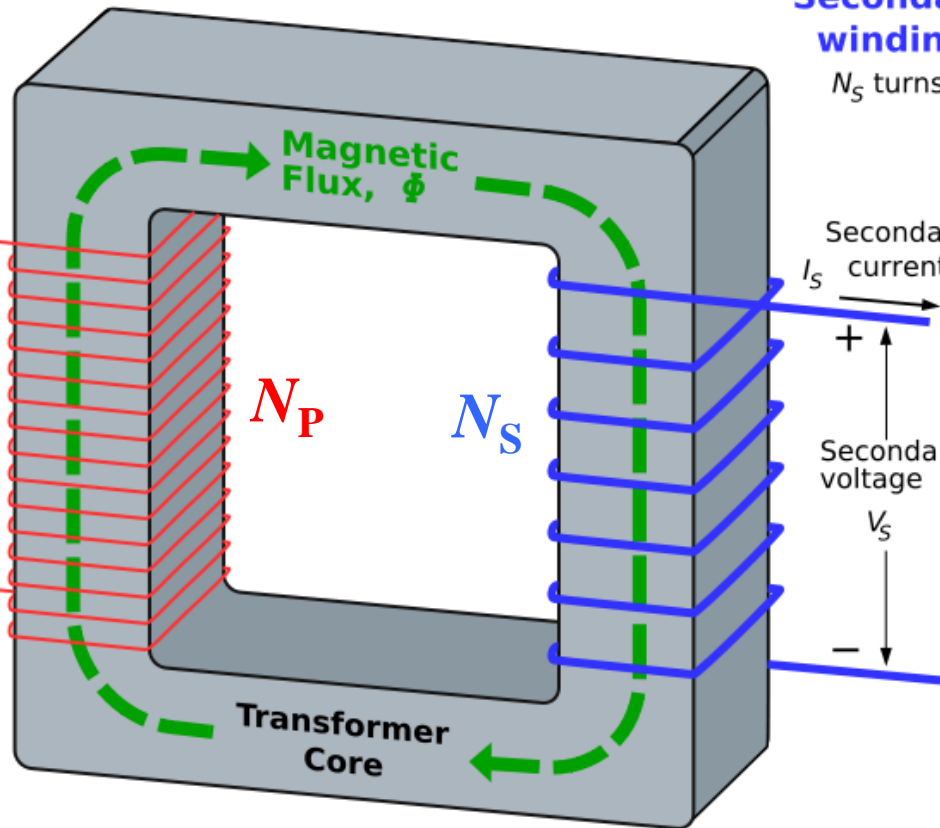

$$\frac{V_S}{V_P} = \frac{N_S}{N_P}$$


Ideal transformer:

$$\frac{V_S}{V_P} = \frac{I_P}{I_S} \Rightarrow \underbrace{V_P \cdot I_P}_{\text{input power}} = \underbrace{V_S \cdot I_S}_{\text{output power}}$$

**Real transformers: the efficiency may reach 97-98%**


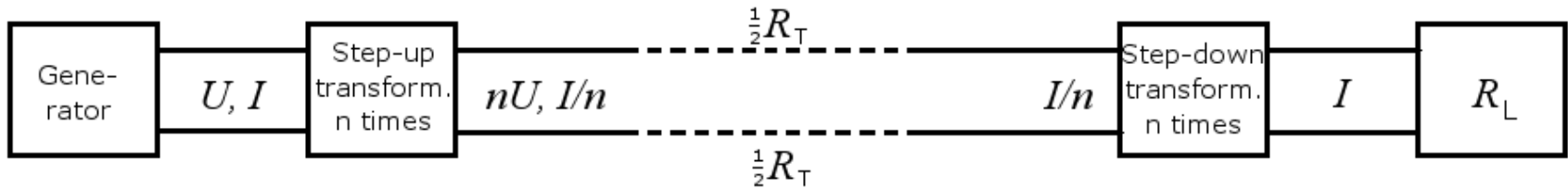
## The same “consumer” as before, but now we use transformers:



Power delivered :  $P_L = R_L \cdot I^2$

Power dissipated:  $P_T = R_T \cdot \left(\frac{I}{n}\right)^2$

Total power sent out :  $P_{\text{total}} = P_L + P_T = \left(R_L + \frac{R_T}{n^2}\right) \cdot I^2$

Efficiency :  $\varepsilon = \frac{P_L}{P_L + P_T} = \frac{R_L}{R_L + \frac{R_T}{n^2}}$

Take, e.g.,  $R_T = R_L$  and  $n = 10$ :

$$\varepsilon = \frac{R_L}{R_L + \frac{R_L}{10^2}} = \frac{R_L}{1.01 \times R_L} \approx 0.99 = 99\%$$

**But the transformers are not 100% efficient; suppose that the efficiency of each one is 97%.**

**Then:**

$$\varepsilon = 0.99 \times (0.97)^2 = 0.93 = 93\%$$

**Without transformers, we had only 50%, and now we have 93%!**


**Transformers give incredible efficiency improvement!**

**Now it's clear why we use all those  
high-voltage transmission lines,  
right?**





# Power grid:

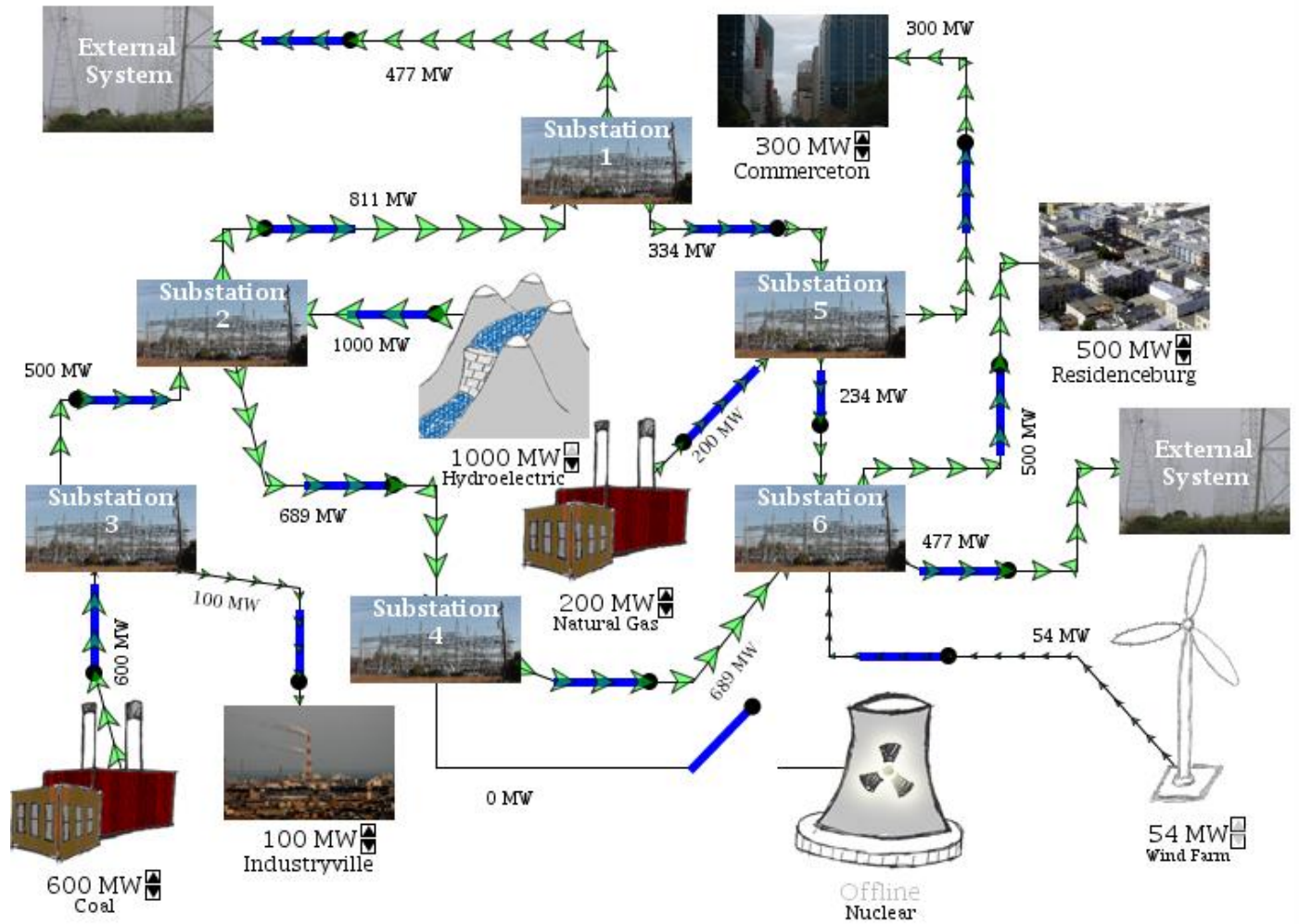

[Java Applet showing how this grid works](#)



[Good Wiki article about the smart grid](#)

[US Department of Labor Web Page](#)

