


Tuesday, 15:00 data (next to Weniger)

Volts across R (Volts)	Current in R (Amps)	Power (Watts)
33.0	0.37	
31.0	0.62	
30.0	0.72	
29.0	0.80	
28.0	0.85	
27.0	0.89	
26.0	0.91	
25.0	0.91	
23.0	0.94	
21.0	0.94	
19.0	0.95	
17.0	0.97	
15.4	0.97	

# Basic theory of real batteries (cells).

①

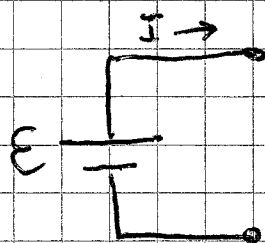1. An ideal cell:  
(ideal voltage source)




The voltage between the terminals is always the same, no matter how much current is taken from the battery:  $E \neq E(I)$


The symbol "E" stands for "Electromotive Force", this term was coined ~200 years ago, when people knew very little about electric currents - and it "stuck", even though it's simply voltage.

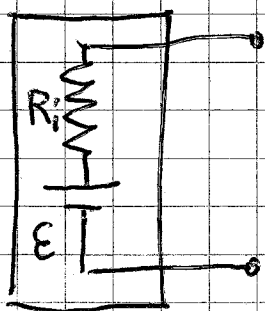2. A real cell:

(real voltage source): it can be thought of as a "black box" containing an ideal voltage source, and a resistor representing the so-called "internal resistance".



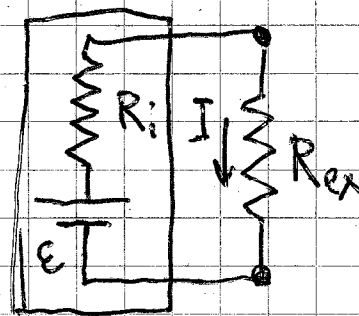So, if you connect an external resistor  $R_{ex}$  to a real voltage source:



the current  $I$  in the resistor is  $I = \frac{E}{R_{Tot}} = \frac{E}{R_i + R_{ex}}$

The ~~voltage~~ voltage across the external resistor is:


$$R_{ex} = \frac{V}{I} \Rightarrow V = R_{ex} \cdot I \\ = \frac{\mathcal{E} \cdot R_{ex}}{R_i + R_{ex}}$$

The power dissipated in the external resistor is:  $P = V \cdot I = \frac{\mathcal{E} \cdot R_{ex}}{R_i + R_{ex}} \cdot \frac{\mathcal{E}}{R_i + R_{ex}} = \mathcal{E}^2 \frac{R_{ex}}{(R_i + R_{ex})^2}$

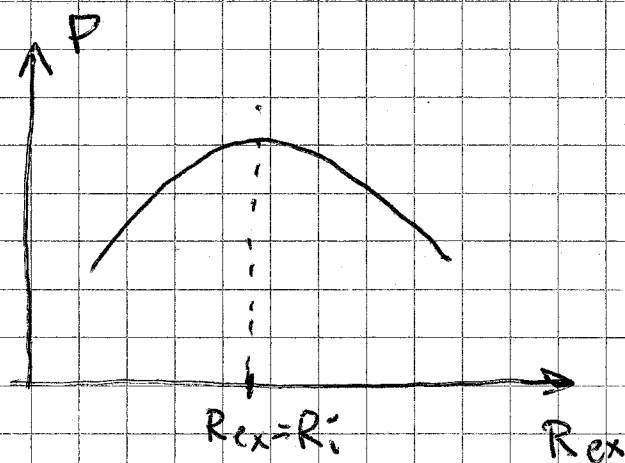Question: If we change  $R_{ex}$ , then, as follows from, the power  $P$  also changes. How does it change?

Does it have a maximum? For which value of  $R_{ex}$ ?


Answer: Yes, it does have a maximum, when the two resistances are equal,  $R_{ex} = R_i$



But, in our experiment, we are interested primarily in determining the maximum power attainable from our PV cell. The question of what is the value of  $R_i$  of the cell is not so important today.

So, if we measure both  $I$  and  $V$  across  $R_{ox}$ , we can obtain  $P$  simply by multiplying the two values:  $P = I \cdot V$

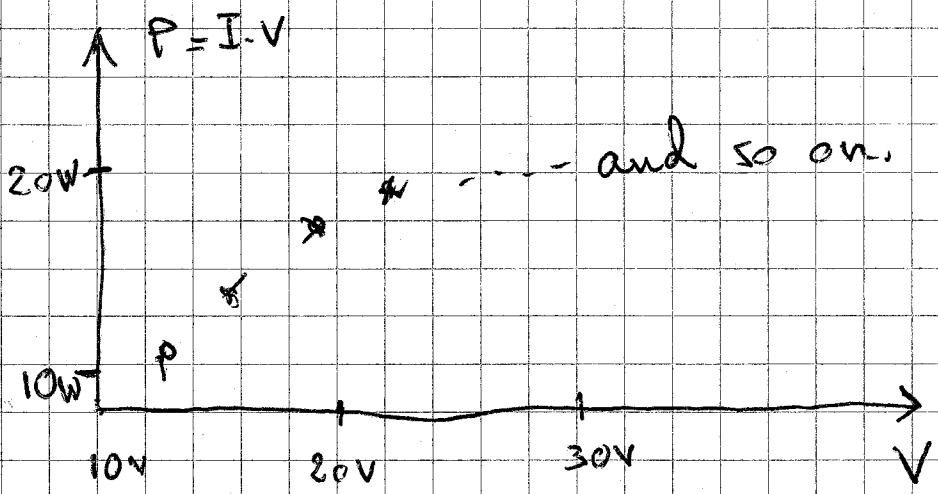Next, plot  $P = I \cdot V$  as a function of  ~~$I$~~   $V$ :



Plot a continuous <sup>(smooth)</sup> curve going through the data points, and find the maximum power.

(4)

If you want to know why the maximum power occurs when  $R_{ex} = R_i$ ?

$P = \mathcal{E}^2 \frac{R_{ex}}{(R_i + R_{ex})^2}$  :  $\mathcal{E}$  and  $R_i$  are constants, so  $P$  is a function of a single variable  $R_{ex}$ .

If  $P(R_{ex})$  has an extremum - minimum or maximum - then at the  $R_{ex}$  value where the extremum occurs, the derivative  $\frac{dP}{dR_{ex}} = 0$

$$\begin{aligned} \frac{dP}{dR_{ex}} &= \mathcal{E}^2 \frac{d}{dR_{ex}} \left[ \frac{R_{ex}}{(R_i + R_{ex})^2} \right] = \\ &= \mathcal{E}^2 \left[ \frac{1}{(R_i + R_{ex})^2} - \frac{2R_{ex}}{(R_i + R_{ex})^3} \right] = \mathcal{E}^2 \frac{R_i - R_{ex}}{(R_i + R_{ex})^3} \end{aligned}$$

This expression is equal zero only if  $R_i = R_{ex}$ .

But is it a maximum, or a minimum?

To find the answer, we have to calculate the second derivative:

$$\frac{d^2P}{dR_{ex}^2} = \frac{d}{dR_{ex}} \left( \frac{dP}{dR_{ex}} \right) = \frac{d}{dR_{ex}} \left[ \mathcal{E}^2 \frac{R_i - R_{ex}}{(R_i + R_{ex})^3} \right]$$

5

$$= \epsilon^2 \left[ -\frac{1}{(R_i + R_{ex})^3} - 3 \frac{(R_i - R_{ex})}{(R_i + R_{ex})^4} \right]$$

$$= \epsilon^2 \left[ \frac{-R_i - R_{ex}}{(R_i + R_{ex})^4} - \frac{3R_i - 3R_{ex}}{(R_i + R_{ex})^4} \right]$$

$$= \epsilon^2 \left[ \frac{-R_i - R_{ex} - 3R_i + 3R_{ex}}{(R_i + R_{ex})^4} \right] = \epsilon^2 \frac{2R_{ex} - 4R_i}{(R_i + R_{ex})^4}$$

At the extremum, where  $R_{ex} = R_i$ , the value of the second derivative is then:

$$\left( \frac{d^2 P}{d R_{ex}^2} \right)_{R_{ex} = R_i} = \epsilon^2 \cdot \frac{-2R_i}{(2R_i)^4} = -\epsilon^2 \frac{1}{8R_i^3}$$

which is a negative value, so that at the extremum there is a maximum

Q.E.D.